




FSM PRIMER

FPGA/VERILOG FROM SCRATCH

DAY 3



C3.1: FSM INTRODUCTION

   Before diving into finite state machines, we need to know what the sequential circuit is?



C3.1: FSM INTRODUCTION

  
- Before diving into finite state machines, we need to know what the sequential circuit is?



*Must know
sequence of
past inputs to
know output*


Sequential circuit

 - Output depends not just on present inputs (as in combinational circuit), but on past sequence of inputs
 - Stores** bits, also known as having “state”
- Simple example: a circuit that counts up in binary




CLOCK SIGNAL

 🖨️ If the sequential circuits need not just current inputs but also the past state of the circuit, then we need to add **storage** and **time** features.



CLOCK SIGNAL

 

X, Y are irrelevant to this slide

🔌 **Clock period:** time interval between pulses

🔌 Above signal: period = 20 ns

🔌 **Clock cycle:** one such time interval


🔌 Above signal shows 3.5 clock cycles

🔌 **Clock frequency:** 1/period

🔌 Above signal: frequency = $1 / 20 \text{ ns} = 50 \text{ MHz}$


🔌 $1 \text{ Hz} = 1/\text{s}$

| Freq | Period |
|---------|---------|
| 100 GHz | 0.01 ns |
| 10 GHz | 0.1 ns |
| 1 GHz | 1 ns |
| 100 MHz | 10 ns |
| 10 MHz | 100 ns |


 


D FLIP-FLOP

 The triangle means
clock input, edge
triggered




  Symbol for rising-edge
triggered D flip-flop




Symbol for falling-edge
triggered D flip-flop

 Internal design: Just
invert servant clock
rather than master






 Is it enough to solve our storage problem?





BASIC REGISTER

   - Typically, we store multi-bit items
 - e.g., storing a 4-bit binary number
- Register.** multiple flip-flops sharing clock signal
 - From this point, we'll use registers for bit storage
 - No need to think of latches or flip-flops
 - But now you know what's inside a register






 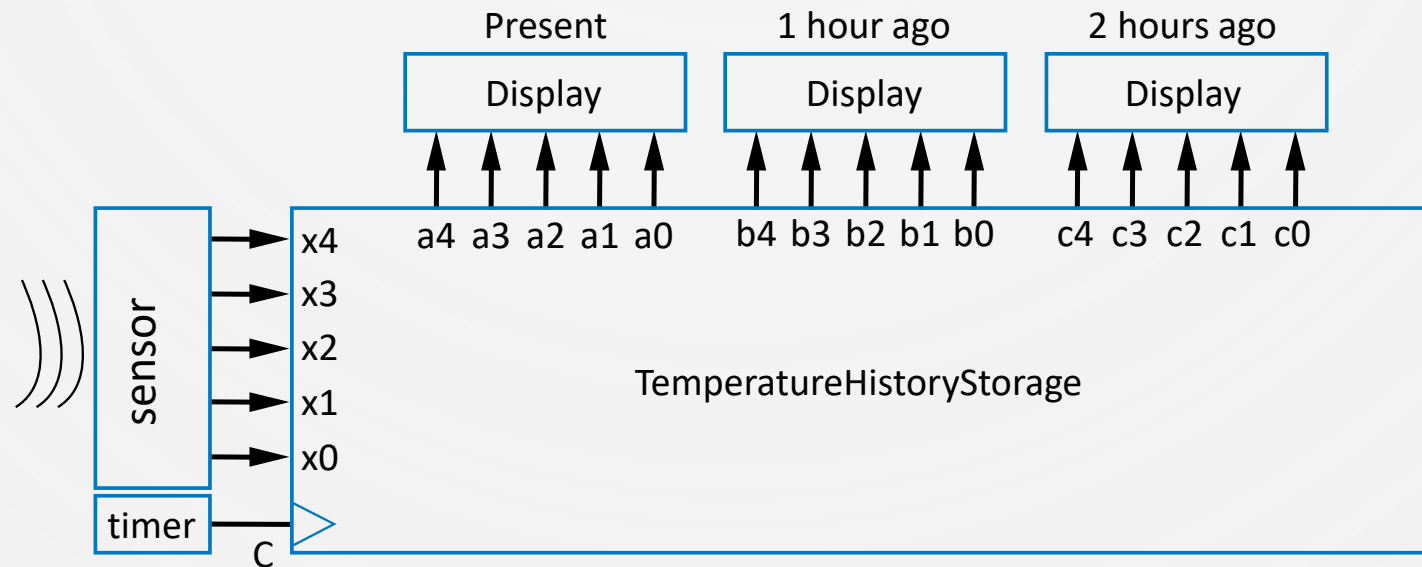EXAMPLE USING REGISTERS: TEMPERATURE DISPLAY

- Temperature history display
 - Sensor outputs temperature as 5-bit binary number
 - Timer pulses C every hour
 - Record temperature on each pulse, display last three recorded values



  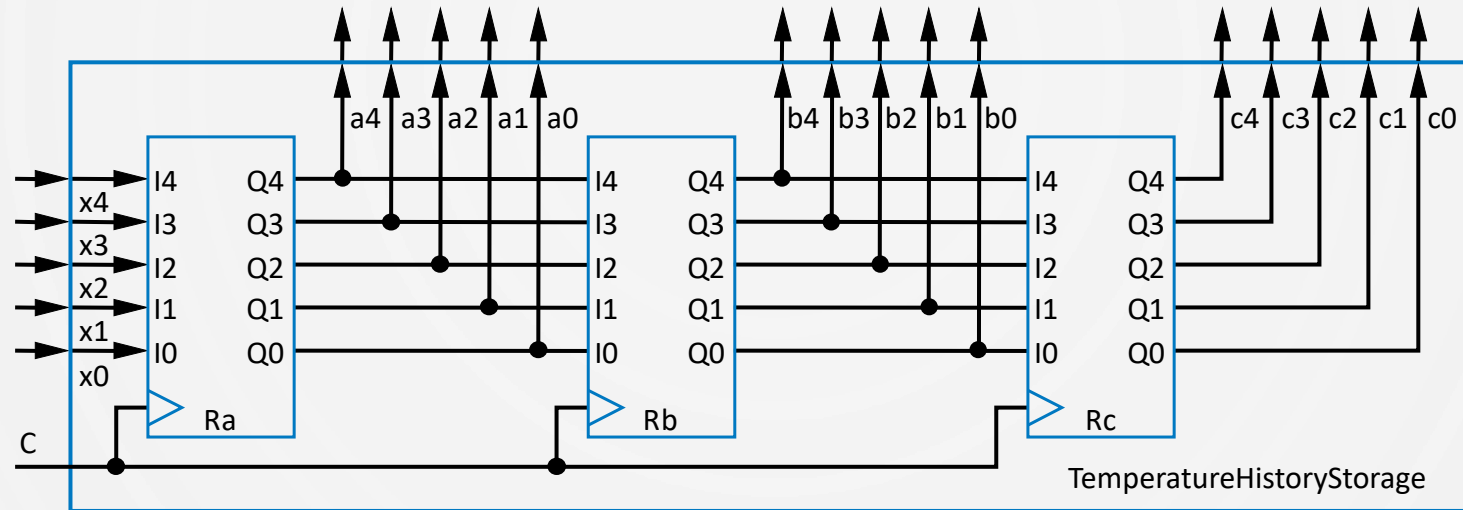EXAMPLE USING REGISTERS: TEMPERATURE DISPLAY



FINITE-STATE MACHINES (FSM)

Want sequential circuit with particular behavior over time

Example: Laser timer




Push button: $x=1$ for 3 clock cycles

How? Let's try three flip-flops

$b=1$ gets stored in first D flip-flop

Then 2nd flip-flop on next cycle, then 3rd flip-flop on next

   OR the three flip-flop outputs, so x should be 1 for three cycles



NEED A BETTER WAY TO DESIGN SEQUENTIAL CIRCUITS

- ❑ Trial and error is not a good design method
 - ❑ Will we be able to “guess” a circuit that works for other desired behavior?
 - ❑ How about counting up from 1 to 9? Pulsing an output for 1 cycle every 10 cycles? Detecting the sequence 1 3 5 in binary on a 3-bit input?
 - ❑ A circuit built by guessing may have undesired behavior
 - ❑ Laser timer: What if press button again while $x=1$? x then stays one another 3 cycles. Is that what we want?
- ❑ Combinational circuit design process had two important things
 1. A formal way to describe desired circuit behavior
 - ❑ Boolean equation, or truth table
 2. A well-defined process to convert that behavior to a circuit
- ❑ We need those things for sequence circuit design





DESCRIBING BEHAVIOR OF SEQUENTIAL CIRCUIT: FSM

Finite-State Machine (FSM)

- A way to describe desired behavior of sequential circuit
 - Akin to Boolean equations for combinational behavior
- List states, and transitions among states
 - Example: Make x change toggle (0 to 1, or 1 to 0) every clock cycle
 - Two states: "Off" ($x=0$), and "On" ($x=1$)
 - Transition from Off to On, or On to Off, on rising clock edge
 - Arrow with no starting state points to initial state (when circuit first starts)

Outputs: x

  

C3.2: FSM EXAMPLES: 0,1,1,1,REPEAT

Want 0, 1, 1, 1, 0, 1, 1, 1, ...




Each value for one clock cycle

Can describe as FSM

Four states



Transition on rising clock edge
to next state

Outputs: x

   

EXTEND FSM TO THREE-CYCLES HIGH LASER TIMER

 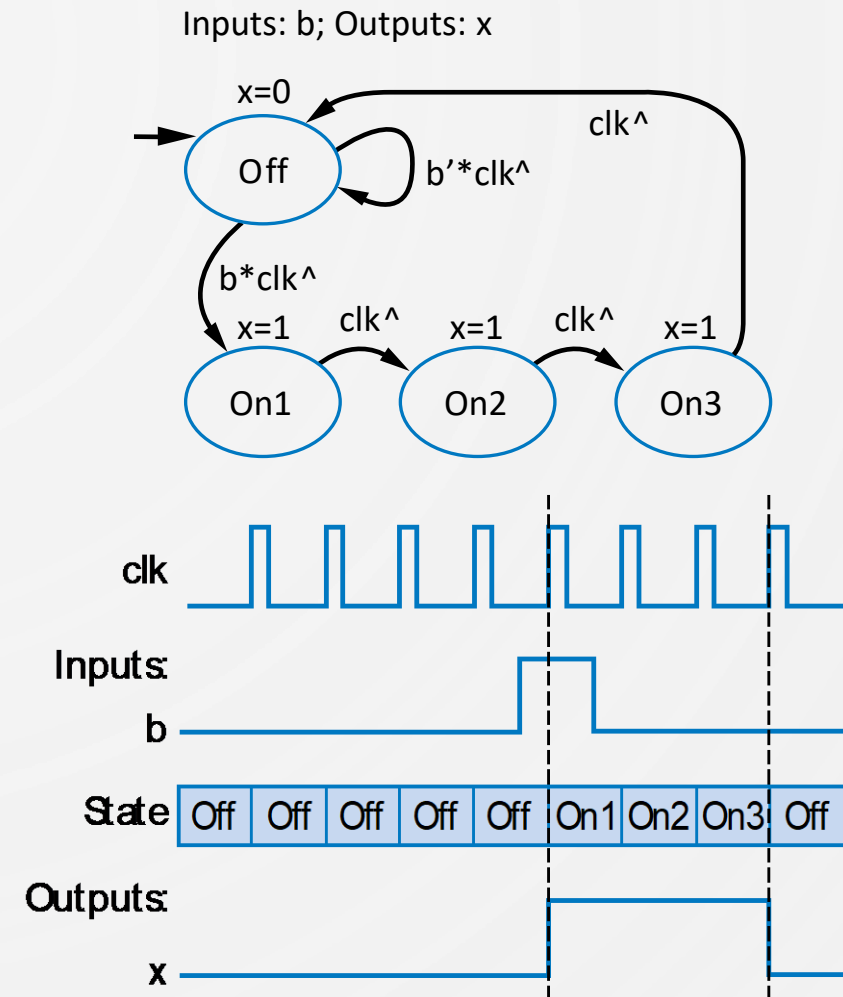- Four states
- Wait in “Off” state while b is 0 (b')
- When b is 1 (and rising clock edge), transition to On1
 - Sets $x=1$
 - On next two clock edges, transition to On2, then On3, which also set $x=1$
- So $x=1$ for three cycles after button pressed



FSM DEFINITION

FSM consists of

- Set of states

- Ex: {Off, On1, On2, On3}

- Set of inputs, set of outputs

- Ex: Inputs: {x}, Outputs: {b}

- Initial state

- Ex: "Off"

- Set of transitions

- Describes next states


- Ex: Has 5 transitions

- Set of actions

- Sets outputs while in states


- Ex: $x=0$, $x=1$, $x=1$, and $x=1$

Inputs: b; Outputs: x

 

We often draw FSM graphically, known as **state diagram**

 
Can also use table (state table), or textual languages



C3.3: FSM DESIGN

Five step design process

| | Step | Description |
|--------|--|---|
| Step 1 | <i>Capture the FSM</i> | Create an FSM that describes the desired behavior of the controller. |
| Step 2 | <i>Create the architecture</i> | Create the standard architecture by using a state register of appropriate width, and combinational logic with inputs being the state register bits and the FSM inputs and outputs being the next state bits and the FSM outputs. |
| Step 3 | <i>Encode the states</i> | Assign a unique binary number to each state. Each binary number representing a state is known as an encoding . Any encoding will do as long as each state has a unique encoding. |
| Step 4 | <i>Create the state table</i> | Create a truth table for the combinational logic such that the logic will generate the correct FSM outputs and next state signals. Ordering the inputs with state bits first makes this truth table describe the state behavior, so the table is a state table. |
| Step 5 | <i>Implement the combinational logic</i> | Implement the combinational logic using any method. |

 

DESIGN EXAMPLE : LASER TIMER EXAMPLE

Step 1: Capture the FSM

Already done

Step 2: Create architecture

2-bit state register (for 4 states)




Input b, output x

Next state signals n1, n0

Step 3: Encode the states

Any encoding with each state unique will work




Inputs: b; Outputs: x

 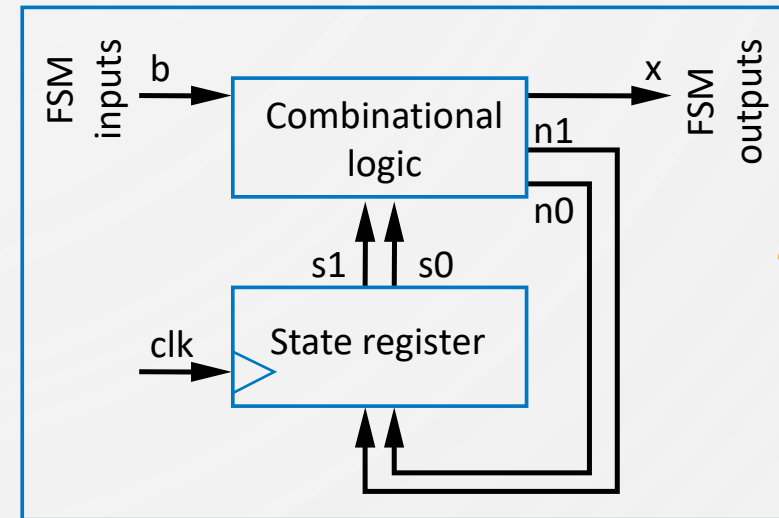 

DESIGN EXAMPLE: LASER TIMER EXAMPLE (CONT)

Step 4: Create state table


| | Inputs | | | Outputs | | |
|------------|--------|----|---|---------|----|----|
| | s1 | s0 | b | x | n1 | n0 |
| <i>Off</i> | 0 | 0 | 0 | 0 | 0 | 0 |
| | 0 | 0 | 1 | 0 | 0 | 1 |
| <i>On1</i> | 0 | 1 | 0 | 1 | 1 | 0 |
| | 0 | 1 | 1 | 1 | 1 | 0 |
| <i>On2</i> | 1 | 0 | 0 | 1 | 1 | 1 |
| | 1 | 0 | 1 | 1 | 1 | 1 |
| <i>On3</i> | 1 | 1 | 0 | 1 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 | 0 |

 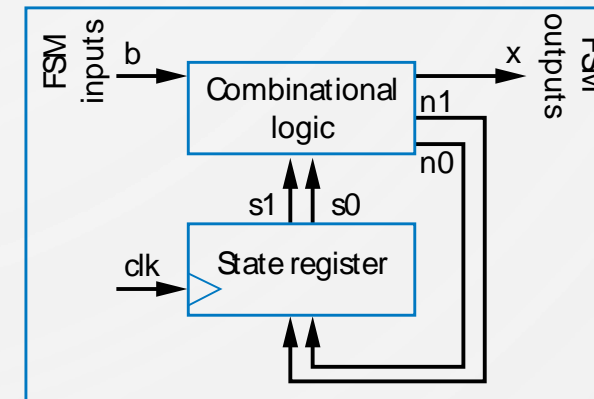 

DESIGN EXAMPLE : LASER TIMER EXAMPLE (CONT)

Step 5: Implement combinational logic

| | Inputs | | | Outputs | | |
|------------|--------|----|---|---------|----|----|
| | s1 | s0 | b | x | n1 | n0 |
| <i>Off</i> | 0 | 0 | 0 | 0 | 0 | 0 |
| | 0 | 0 | 1 | 0 | 0 | 1 |
| <i>On1</i> | 0 | 1 | 0 | 1 | 1 | 0 |
| | 0 | 1 | 1 | 1 | 1 | 0 |
| <i>On2</i> | 1 | 0 | 0 | 1 | 1 | 1 |
| | 1 | 0 | 1 | 1 | 1 | 1 |
| <i>On3</i> | 1 | 1 | 0 | 1 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 | 0 |

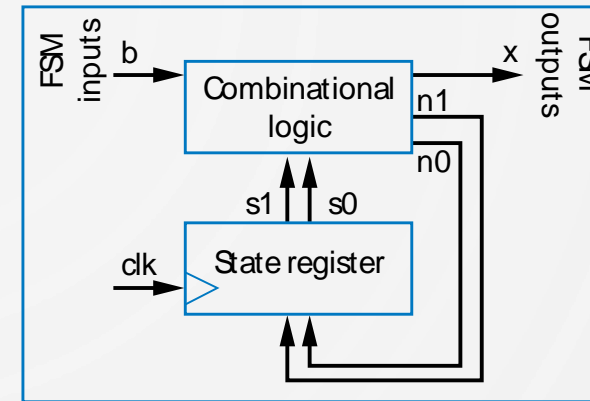


$$x = s1 + s0 \text{ (note from the table that } x=1 \text{ if } s1 = 1 \text{ or } s0 = 1 \text{)}$$

$$n1 = s1's0b' + s1's0b + s1s0'b' + s1s0'b$$

$$n1 = s1's0 + s1s0'$$

$$n0 = s1's0'b + s1s0'b' + s1s0'b$$


$$n0 = s1's0'b + s1s0'$$

 

DESIGN EXAMPLE : LASER TIMER EXAMPLE (CONT)

Step 5: Implement combinational logic (cont)


| | Inputs | | | Outputs | | |
|------------|--------|----|---|---------|----|----|
| | s1 | s0 | b | x | n1 | n0 |
| <i>Off</i> | 0 | 0 | 0 | 0 | 0 | 0 |
| | 0 | 0 | 1 | 0 | 0 | 1 |
| <i>On1</i> | 0 | 1 | 0 | 1 | 1 | 0 |
| | 0 | 1 | 1 | 1 | 1 | 0 |
| <i>On2</i> | 1 | 0 | 0 | 1 | 1 | 1 |
| | 1 | 0 | 1 | 1 | 1 | 1 |
| <i>On3</i> | 1 | 1 | 0 | 1 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 | 0 |

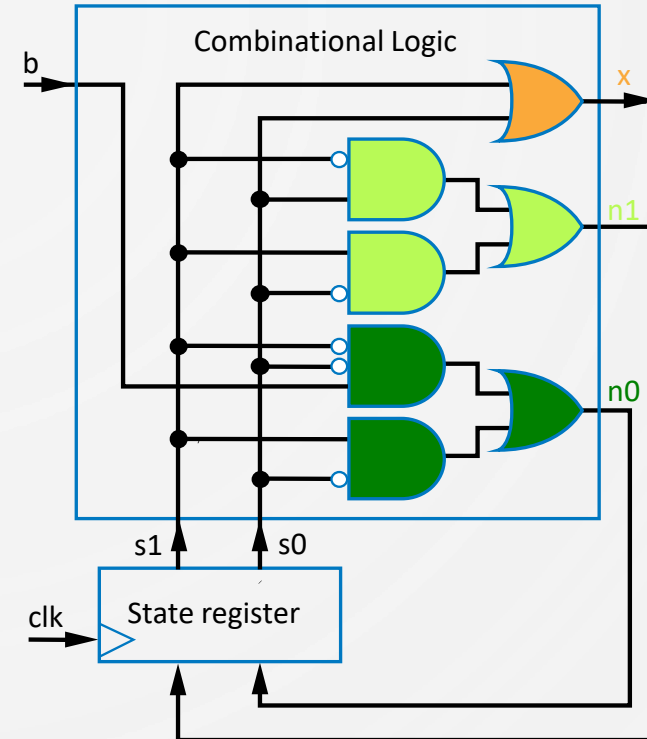

$$x = s1 + s0$$




$$n1 = s1's0 + s1s0'$$

$$n0 = s1's0'b + s1s0'$$

 

DESIGN EXAMPLE: SEQUENCE GENERATOR

 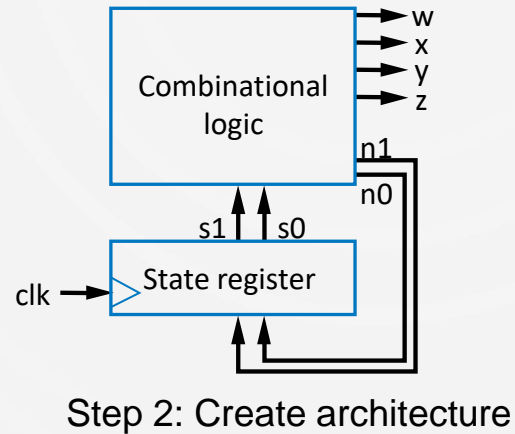 - Want generate sequence 0001, 0011, 1100, 1000, (repeat)
- Each value for one clock cycle. e.g., to control magnets of a “stepper motor”



| Inputs | | Outputs | | | | | |
|--------|----|---------|---|---|---|----|----|
| s1 | s0 | w | x | y | z | n1 | n0 |
| A | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| B | 0 | 0 | 0 | 1 | 1 | 1 | 0 |
| C | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| D | 1 | 1 | 0 | 0 | 0 | 0 | 0 |

Step 4: Create state table

$$\begin{aligned}
 w &= s1 \\
 x &= s1s0' \\
 y &= s1's0 \\
 z &= s1' \\
 n1 &= s1 \text{ xor } s0 \\
 n0 &= s0'
 \end{aligned}$$

